

### MESSAGE DISPLAY ON LCD

C3	C2
22P	22P

VR1  
10K

8MH

XTAL

+



IC1

ATmega8535

R1  
4.7K

PS

$$-5V+$$

Fig. 10: Component layout for the PCB in Fig. 9